



K23P 3102

Reg. No. :

Name :

**I Semester M.Sc. Degree (C.B.C.S.S. – OBE – Regular)
Examination, October 2023
(2023 Admission)
PHYSICS
MSPHY01C04 – Electronics**

Time : 3 Hours

Max. Marks : 60

SECTION – A

Answer any 5, each one carries 3 marks :

1. What are the characteristics of an ideal opamp ? Explain perfect balance.
2. Define the following basic opamp parameters. Give their typical values :
 - a) Input offset voltage
 - b) Input bias current
 - c) Input offset current.
3. Distinguish between :
 - a) Active filter and passive filter
 - b) Low pass, High pass, Band pass and Band reject filters
 - c) Butterworth filter and Chebyshev filter.
4. What are opamp comparators ? Explain the working of a ZCD. Why it is called so ?
5. Explain the following in a microprocessor and give their importance :
 - a) ALE
 - b) $\text{IO}/\overline{\text{M}}$
 - c) S_1 and S_0
6. What are flip-flops ? Explain its use as a memory element with suitable example.

P.T.O.



SECTION – B

Answer **any 3, each one** carries **6** marks :

7. Describe the working of a three-input scaling amplifier. Design and construct an inverting scaling amplifier with output $0.5 V_1 + 2V_2 + V_3$. Sketch the output if $V_1 = -2V$ DC, $V_2 = 1V$ DC and $V_3 = 2 \sin(100\pi t)$.
8. Determine the output voltage of an opamp for input voltages $V_1 = 1050 \mu V$, $V_2 = 950 \mu V$. Given the opamp has a differential gain $A_d = 1000$ and CMRR = 100 dB. What will be the result if the input voltages V_1 and V_2 are respectively $50 \mu V$ and $150 \mu V$? Comment on your answer.
9. Design and construct a first order low pass Butterworth filter of high cut off frequency of 3 KHz.
10. Design and implement an asynchronous decade counter using T flip-flops.
11. An 8-bit DAC has an output of 0.05 V for a digital input of 00000001. Determine :
 - i) Step size
 - ii) Full scale output
 - iii) Resolution
 - iv) Output voltage for an input of 00101100.

SECTION – C

Answer **any 3, each one** carries **9** marks :

12. Discuss the four closed loop configurations of opamp using block diagram representation. Analyse the voltage series feedback amplifier and evaluate closed loop :
 - i) Voltage gain
 - ii) Input resistance
 - iii) Output resistance and
 - iv) Bandwidth.



13. Describe the frequency response of a non-compensated opamp. Obtain the transfer function and analyse the high frequency equivalent of an opamp with single break frequency. How the stability of such amplifiers can be analysed ?

14. With the relevant schematic diagrams Explain the working of :

i) Astable Multivibrator and

ii) Schmitt Trigger.

Explain the hysteresis in Schmitt trigger.

15. What are shift registers ? Which are the general data transmission scheme in them ? Explain any three among them in detail.

16. With the help of a block diagram discuss the internal architecture of intel 8085.

